

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2021****Subject Code:3170916****Date:15/12/2021****Subject Name:Advanced Electric Drives****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|---|-----------|
| Q.1 | (a) State in brief, how torque is estimated in closed loop control of electric drives. | 03 |
| | (b) Explain in brief, the control of Current Source Inverter with necessary diagram. | 04 |
| | (c) Explain PWM converter as line side rectifier with necessary figure. | 07 |
| Q.2 | (a) Describe Selected Harmonic Elimination with necessary figure. | 03 |
| | (b) Draw the block diagram of Electric drive and explain each block in brief. | 04 |
| | (c) Explain operation of H bridge as a 4-Q drive. | 07 |
| | OR | |
| | (c) Draw and explain the equivalent circuit of a single –phase induction machine. | 07 |
| Q.3 | (a) State advantages of vector control over scalar control. | 03 |
| | (b) Compare VSI and CSI fed drives. | 04 |
| | (c) Write a note on Reference-frame theory, and state commonly used reference frames. | 07 |
| | OR | |
| Q.3 | (a) Compare DTC and FOC | 03 |
| | (b) Discuss what will happen if V/f ratio is not kept constant in IM drive. | 04 |
| | (c) Draw and explain operation of open loop V/f control of Induction motor with PWM voltage fed converter. | 07 |
| Q.4 | (a) List different permanent magnet motors. | 03 |
| | (b) Draw block diagram of synchronous motor drive. | 04 |
| | (c) Explain direct torque control of synchronous motor. | 07 |
| | OR | |
| Q.4 | (a) Draw block diagram for closed loop speed control of SRM. | 03 |
| | (b) List different control techniques of PMSM. | 04 |
| | (c) Explain CSI fed synchronous motor drives. | 07 |
| Q.5 | (a) List various topologies of SRM drives. | 03 |
| | (b) Discuss PWM module in DSP. | 04 |
| | (c) State the eight different possible switching vectors in SVM with diagram. Describe sectors in the same. | 07 |
| | OR | |
| Q.5 | (a) Draw figure showing construction of any one type of BLDC motor. | 03 |
| | (b) Write a short note on TMSLF2407 with reference to motion control. | 04 |
| | (c) State names of some DSPs used in motion control and discuss the use of same. | 07 |

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – SUMMER 2022****Subject Code:3170916****Date:08/06/2022****Subject Name:Advanced Electric Drives****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|--|-----------|
| Q.1 | (a) Explain PWM control of inverter in brief. | 03 |
| | (b) Draw the block diagram of Electric drive. | 04 |
| | (c) Draw and explain PWM converter as line side rectifier. | 07 |
| Q.2 | (a) Describe Selected Harmonic Elimination with necessary figure. | 03 |
| | (b) Discuss the importance of V/f ratio in IM drive. | 04 |
| | (c) Describe the operation of H bridge as a 4-Q drive. | 07 |
| | OR | |
| | (c) Write a note on reference frame theory. | 07 |
| Q.3 | (a) State advantages of SHE technique. | 03 |
| | (b) Compare vector control and scalar control. | 04 |
| | (c) Discuss speed control in BLDC motors. | 07 |
| | OR | |
| Q.3 | (a) Describe use of DSP to generate PWM. | 03 |
| | (b) Compare Direct Torque Control and Field Oriented Control. | 04 |
| | (c) Draw and explain operation of open loop V/f control of Induction motor with PWM voltage fed converter. | 07 |
| Q.4 | (a) List different permanent magnet motors. | 03 |
| | (b) Draw block diagram of synchronous motor drive. | 04 |
| | (c) Explain direct torque control of synchronous motor. | 07 |
| | OR | |
| Q.4 | (a) Draw block diagram for closed loop speed control of SRM. | 03 |
| | (b) List different control techniques of PMSM. | 04 |
| | (c) List and explain various topologies for SRM drives. | 07 |
| Q.5 | (a) Compare open loop and close loop control of an electric drive. | 03 |
| | (b) Draw equivalent circuit model of Induction motor. | 04 |
| | (c) Explain switching vectors in space vector modulation with a neat labelled diagram. | 07 |
| | OR | |
| Q.5 | (a) State advantages and drawbacks of PM motors. | 03 |
| | (b) Draw figure showing construction of outer rotor design type BLDC motor. | 04 |
| | (c) Draw block diagram for DSP based Brushless Direct Current Motor Drive System. | 07 |