

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2021****Subject Code:3170906****Date:15/12/2021****Subject Name:Advanced Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		<b>MARKS</b>
<b>Q.1</b>	(a) With block diagram Compare Linear voltage regulator and Switch mode voltage regulator.	<b>03</b>
	(b) Write the advantages of resonance converter as compared to PWM converter.	<b>04</b>
	(c) Derive output equation for the buck-boost converter with necessary	<b>07</b>
<b>Q.2</b>	(a) What is the need of Resonant Converter? Compare Series Loaded Resonant (SLR) converter with Parallel loaded resonant (PLR) Converter	<b>03</b>
	(b) Differentiate between continuous mode of conduction and discontinuous mode of conduction.	<b>04</b>
	(c) Justify the name of converter as zero voltage switching converter with necessary diagram and waveform.	<b>07</b>
	<b>OR</b>	
	(c) Illustrate how the harmonic current are canceled by phase shifting transformer in 12 pulse rectifier.	<b>07</b>
<b>Q.3</b>	(a) Compare the three topologies of multilevel inverter.	<b>03</b>
	(b) What are the advantages of cascaded H bridge multi-level inverter over other two topologies?	<b>04</b>
	(c) Explain the operation of zero voltage switching resonant converter with circuit diagram, waveform and required equation.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Compare zero voltage switching (ZVS) and zero current switching (ZCS) resonant converter.	<b>03</b>
	(b) Explain the operation of Class E converter	<b>04</b>
	(c) Explain the operation of 5-Level DCMLI. Also discuss problems associated with DCMLI and how it will overcome.	<b>07</b>
<b>Q.4</b>	(a) Classification Of FACTS devices.	<b>03</b>
	(b) Draw the one-line diagram of HVDC & Discuss the equipments of HVDC systems.	<b>04</b>
	(c) Explain following transformer connection with phasor diagram used in multi pulse converter. (a) Y-Z1 (b) Δ-Z1	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) State the need of reactive power compensation.	<b>03</b>
	(b) Explain the working of Fixed Capacitor Thyristor-Controlled Reactor (FC-TCR). Draw neat diagrams.	<b>04</b>
	(c) Discuss operation of five level flying capacitor multilevel inverter with neat circuit diagram and waveforms.	<b>07</b>
<b>Q.5</b>	(a) Draw schematic diagram of Monopolar, Bipolar and Homopolar link.	<b>03</b>
	(b) State advantages and limitation of SSSC.	<b>04</b>

- (c) The class E resonance inverter operates at resonance and has  $V_s = 12$  V,  $R = 10\ \Omega$ ,  $f_s = 25$  kHz and  $Q = 7$ . Determine optimum value of L, C,  $C_e$  and  $L_e$ . **07**

**OR**

- Q.5** (a) Give classification and applications of phase shifting transformer. **03**  
(b) State advantages and limitation of SSSC. **04**  
(c) Discuss operation of Flyback converter. Draw its circuit diagram and waveforms. **07**

\*\*\*\*\*

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – SUMMER 2022****Subject Code:3170906****Date:08/06/2022****Subject Name:Advanced Power Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- |            |   |           |
|------------|---|-----------|
| <b>Q.1</b> | (a) Give comparison between continuous conduction mode and discontinuous conduction mode.   | <b>03</b> |
|            | (b) Discuss static characteristics of SVC.  | <b>04</b> |
|            | (c) Derive output equation for the buck-boost converter with necessary.   | <b>07</b> |
| <b>Q.2</b> | (a) Discuss multi output switch mode regulators.  | <b>03</b> |
|            | (b) What is the need of Resonant Converter? Compare Series Loaded Resonant (SLR) converter with Parallel loaded resonant (PLR) Converter. | <b>04</b> |
|            | (c) Discuss discontinuous mode of operation in buck boost converter with waveforms.   | <b>07</b> |
| <b>OR</b>  |   |           |
|            | (c) Explain zero current switching dc-dc converter.   | <b>07</b> |
| <b>Q.3</b> | (a) Explain the concept & need of Multi Level Inverter (MLI)  | <b>03</b> |
|            | (b) What are the advantages of cascaded H bridge multi-level inverter over other two topologies?  | <b>04</b> |
|            | (c) Explain the operation of zero voltage switching resonant converter with circuit diagram, waveform and required equation.              | <b>07</b> |
| <b>OR</b>  |   |           |
| <b>Q.3</b> | (a) Draw schematic diagram of 12 pulse converter with transformer connection.   | <b>03</b> |
|            | (b) Discuss difference between series and shunt compensation.   | <b>04</b> |
|            | (c) Discuss sine PWM techniques used for multilevel inverter.   | <b>07</b> |
| <b>Q.4</b> | (a) Classification Of FACTS devices.  | <b>03</b> |
|            | (b) Discuss need of phase shifting transformer.   | <b>04</b> |
|            | (c) Explain following transformer connection with phasor diagram used in multi pulse converter. (a) Y-Z1 (b) Δ-Z1                         | <b>07</b> |
| <b>OR</b>  |   |           |
| <b>Q.4</b> | (a) Discuss static synchronous series compensator.  | <b>03</b> |
|            | (b) Give comparison of HVAC and HVDC transmission.  | <b>04</b> |
|            | (c) Explain the operation of six pulse diode rectifier with resistive load with necessary diagram and waveform.                           | <b>07</b> |
| <b>Q.5</b> | (a) Explain working principal of SSSC.  | <b>03</b> |
|            | (b) Comparison of SVC & STATCOM.  | <b>04</b> |
|            | (c) Discuss operation of Flyback converter. Draw its circuit diagram and waveforms.   | <b>07</b> |

**OR**

- |            |            |  |           |
|------------|------------|--|-----------|
| <b>Q.5</b> | <b>(a)</b> | What is the need of Reactive Power Compensation?                     | <b>03</b> |
|            | <b>(b)</b> | State advantages and limitation of SSSC.                             | <b>04</b> |
|            | <b>(c)</b> | Explain operating principle of Unified power flow controller (UPFC). | <b>07</b> |

\*\*\*\*\*